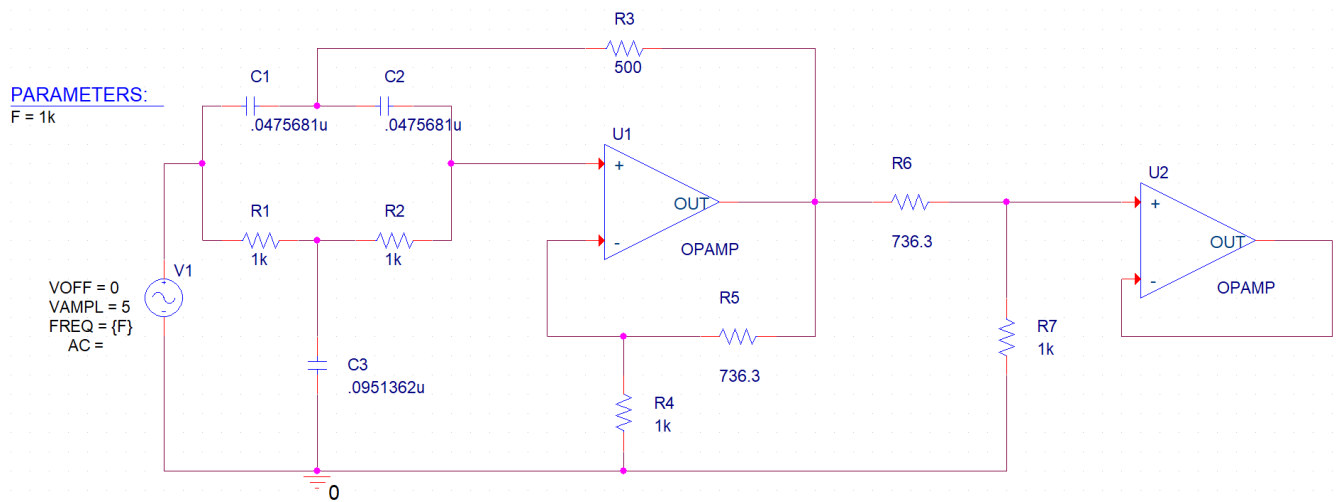


ECE 2101L Lab #9

Band Stop Filter



Kyler Martinez and Daniel Ruiz – Group 2

December 11th, 2020

Objective

The objective of the lab is to explore band stop filters and the magnitude responses that they produce, as well as be able to find the transfer function of a circuit designed to produce a band stop response.

Materials

The necessary equipment needed for the lab are as follows

1. Breadboard
2. 4 BNC Clip Connectors
3. Clip Leads
4. 2 $.0475681\mu\text{F}$ and one $.0951362\mu\text{F}$ Capacitor
5. 4 $1\text{k}\Omega$, 2 736.3Ω , and one 500Ω Resistors
6. 2 Op Amps
7. LCR Meter
8. Digital Multimeter
9. Oscilloscope
10. Function Generator

Pre-Lab

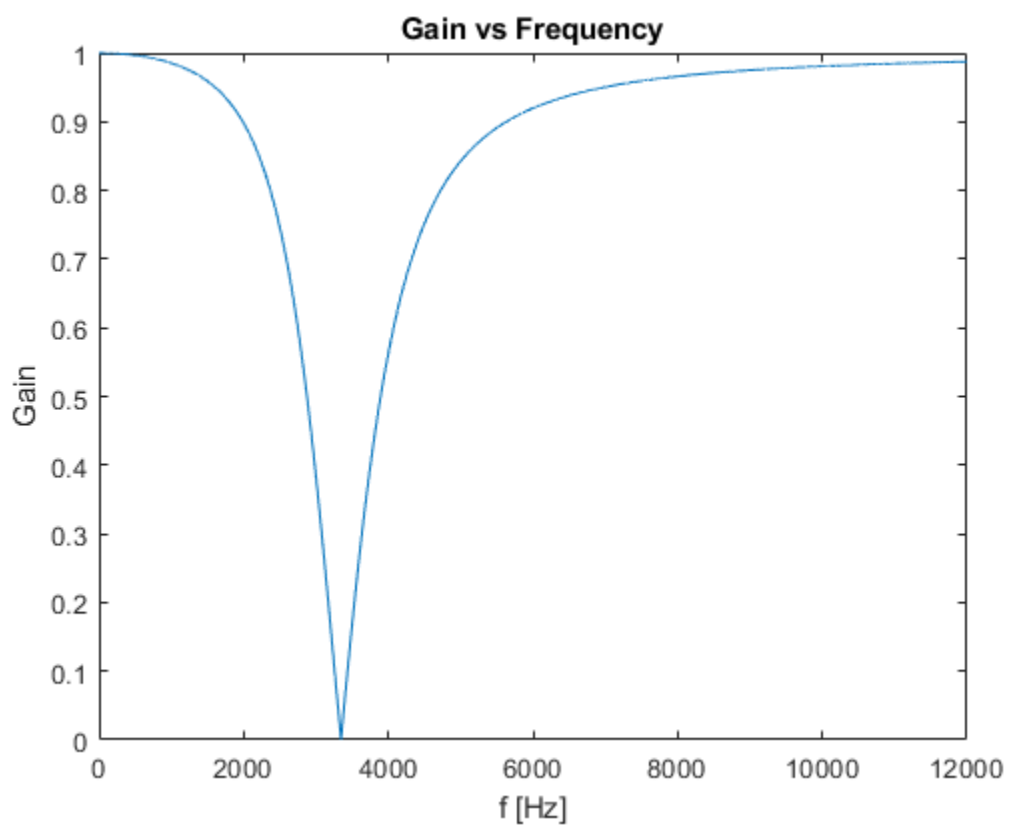


Figure 1: MATLAB Plot

Procedure

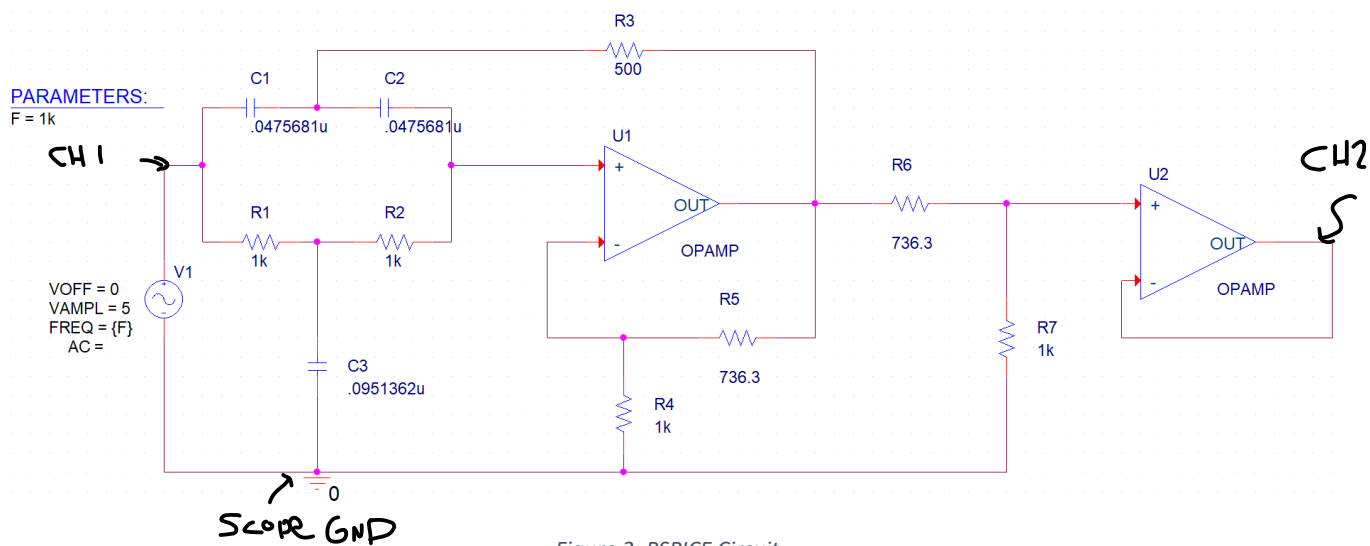


Figure 2: PSpice Circuit


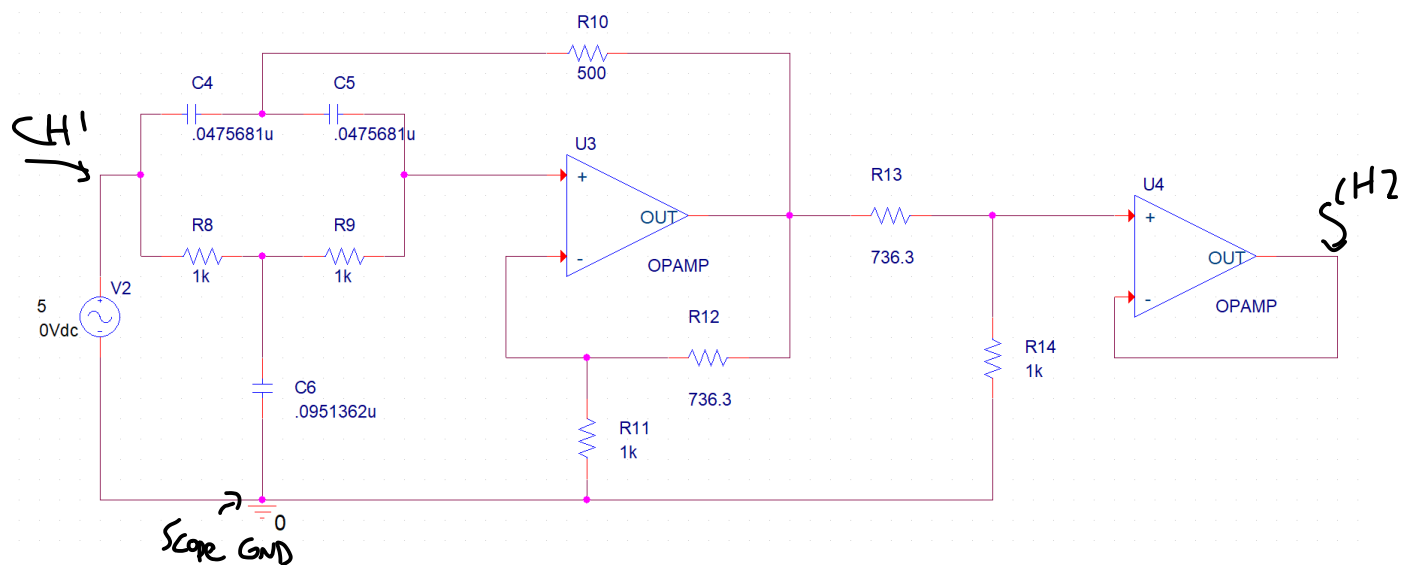
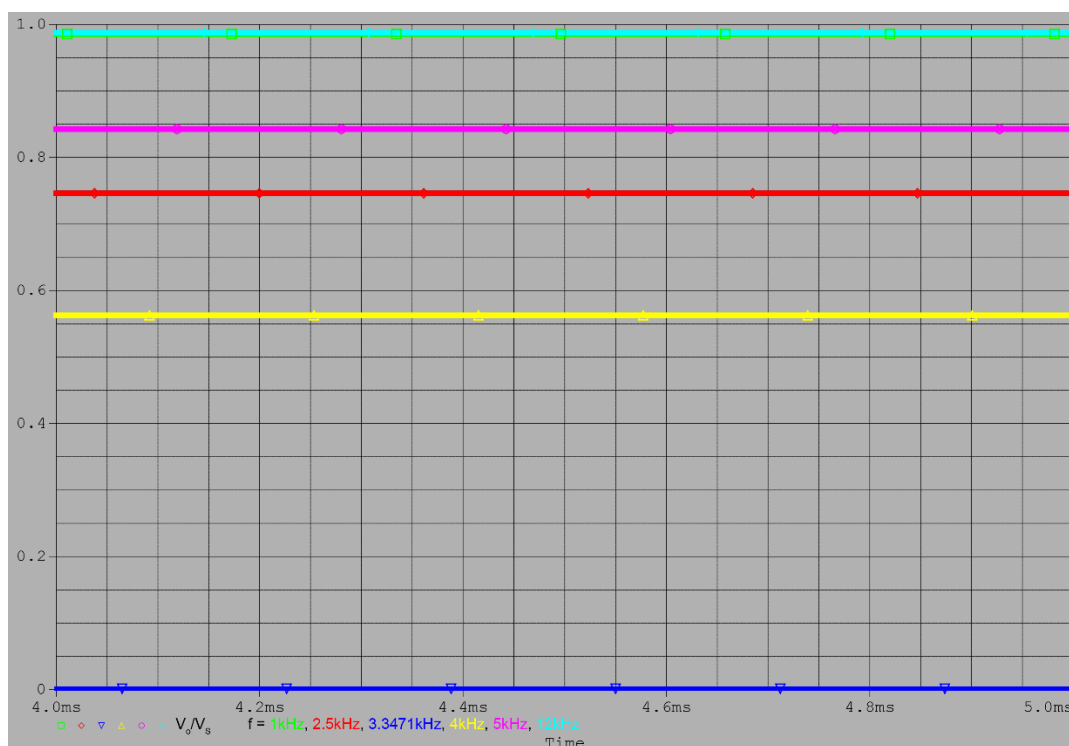


Figure 3: PSpice Circuit For Magnitude Response (Post Lab)

Results

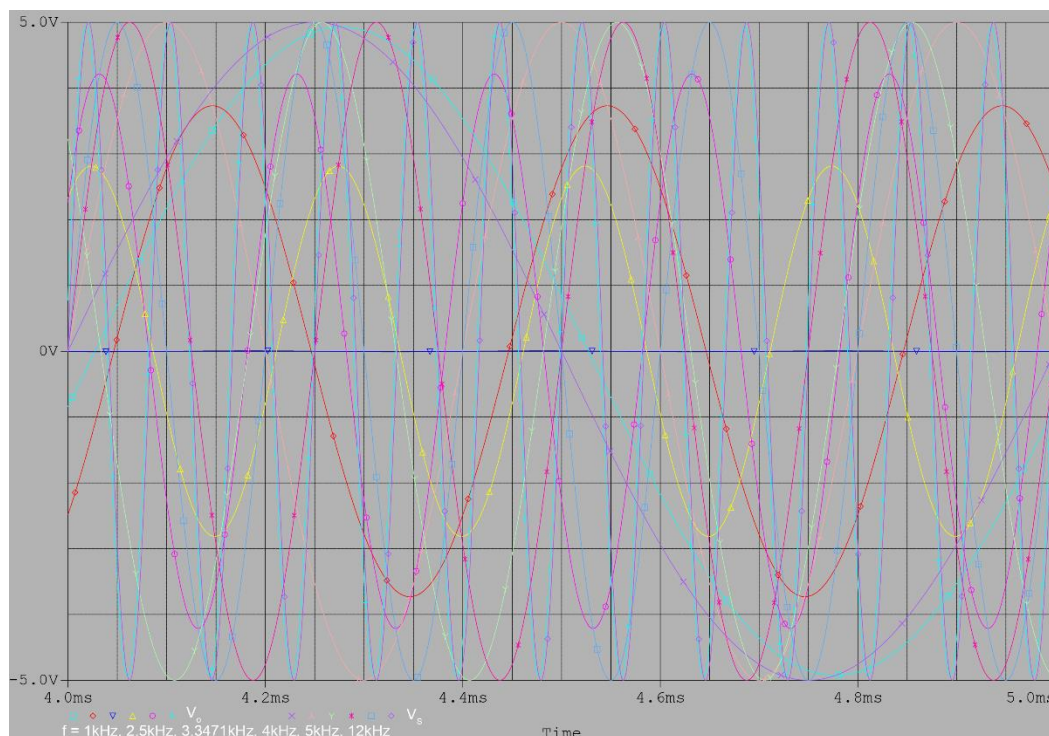

CURSOR 1,2	$\text{MAX}(V(U2:OUT))/\text{MAX}(V(V1:+))$	985.345m
	$\text{MAX}(V(U2:OUT))/\text{MAX}(V(V1:+))$	746.182m
	$\text{MAX}(V(U2:OUT))/\text{MAX}(V(V1:+))$	707.376m
	$\text{MAX}(V(U2:OUT))/\text{MAX}(V(V1:+))$	1.4366m
	$\text{MAX}(V(U2:OUT))/\text{MAX}(V(V1:+))$	562.762m
	$\text{MAX}(V(U2:OUT))/\text{MAX}(V(V1:+))$	705.626m
	$\text{MAX}(V(U2:OUT))/\text{MAX}(V(V1:+))$	842.613m
	$\text{MAX}(V(U2:OUT))/\text{MAX}(V(V1:+))$	987.523m

Figure 6: Measurement For Magnitude For Various Frequencies

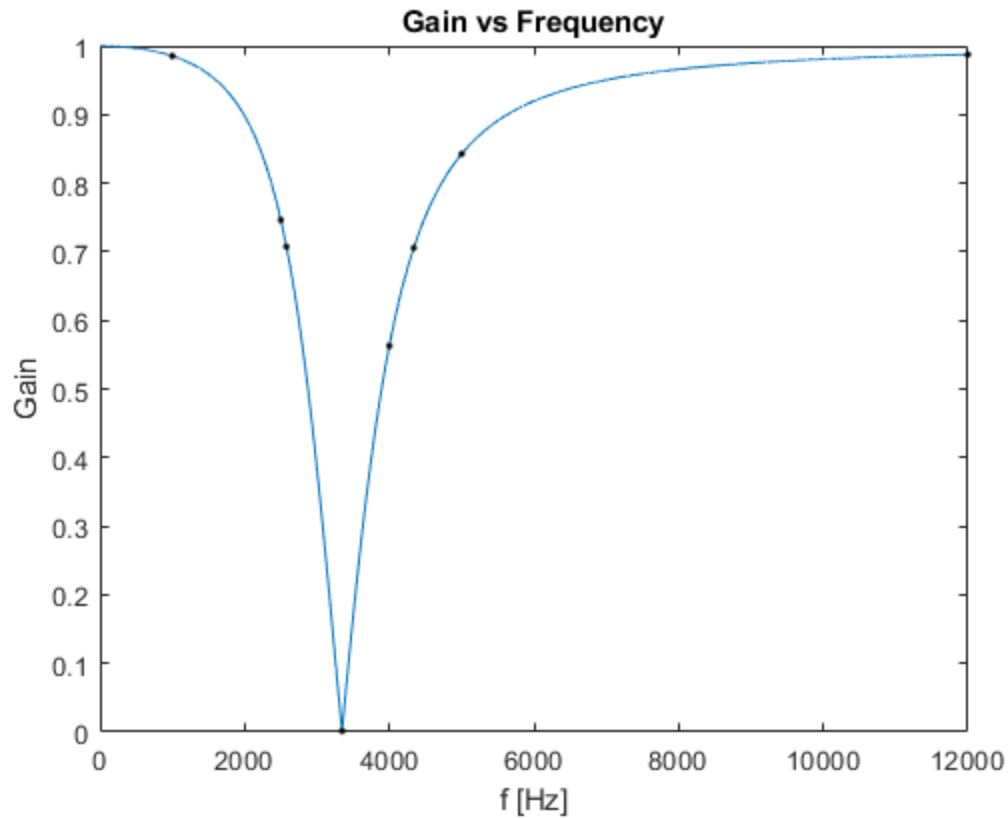


Figure 7: MATLAB Plot With Data In Black

Data Table For Frequencies & Corresponding Gain


f [Hz]	$ H(j*2*\pi) $
1k	985.345m
2.5k	746.182m
2.5774k	707.376m
3.3471k	1.4366m
4k	562.762m
4.3379k	705.626m
5k	842.613m
12k	987.523m

Analysis

We can see from our data that as we increase the frequency the gain decreases until $f = 3.3471\text{kHz}$, where the gain is incredibly small, about .0014, which is close enough to 0 for practical purposes. The gain then increases once more as we increase the frequency past this stopping point. The 3dB frequencies were found at about 2.5774kHz and 4.3379kHz and the band width of the filter would be $0\text{Hz} < f <= 2.5774\text{kHz}$ and $4.3379\text{kHz} <= f$. Our data closely matches the theoretical magnitude response since we used PSPICE to collect our data which is heavily based on theoretical calculations.

Problems

a.

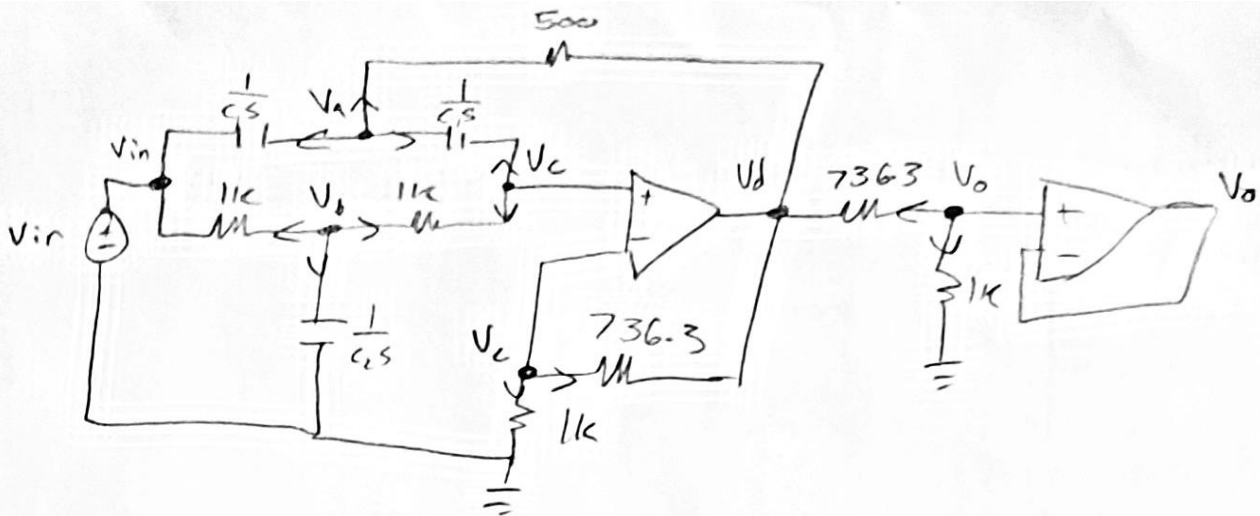

$$C_1 = .0475681\ \mu\text{F} \quad C_2 = .0951362\ \mu\text{F}$$

$$(a) \quad \frac{V_a - V_{in}}{\frac{1}{c_1s}} + \frac{V_a - V_c}{\frac{1}{c_1s}} + \frac{V_a - V_d}{500} = 0$$

$$(b) \quad \frac{V_b - V_{in}}{1\text{k}} + \frac{V_b - V_c}{1\text{k}} + \frac{V_b}{\frac{1}{c_2s}} = 0$$

$$(c_1) \quad \frac{V_c - V_a}{\frac{1}{c_1s}} + \frac{V_c - V_b}{1\text{k}} = 0$$

$$(c_2) \quad \frac{V_c - V_d}{736.3} + \frac{V_c}{1\text{k}} = 0$$

$$(d) \quad \frac{V_o - V_d}{736.3} + \frac{V_o}{1\text{k}} = 0$$

$$H(s) = \frac{s^2 + 441900000}{s^2 + 11090s + 441900000}$$

b. Write a Spice program to find the magnitude of the transfer function of your circuit. Run your program and compare with your experimental results.

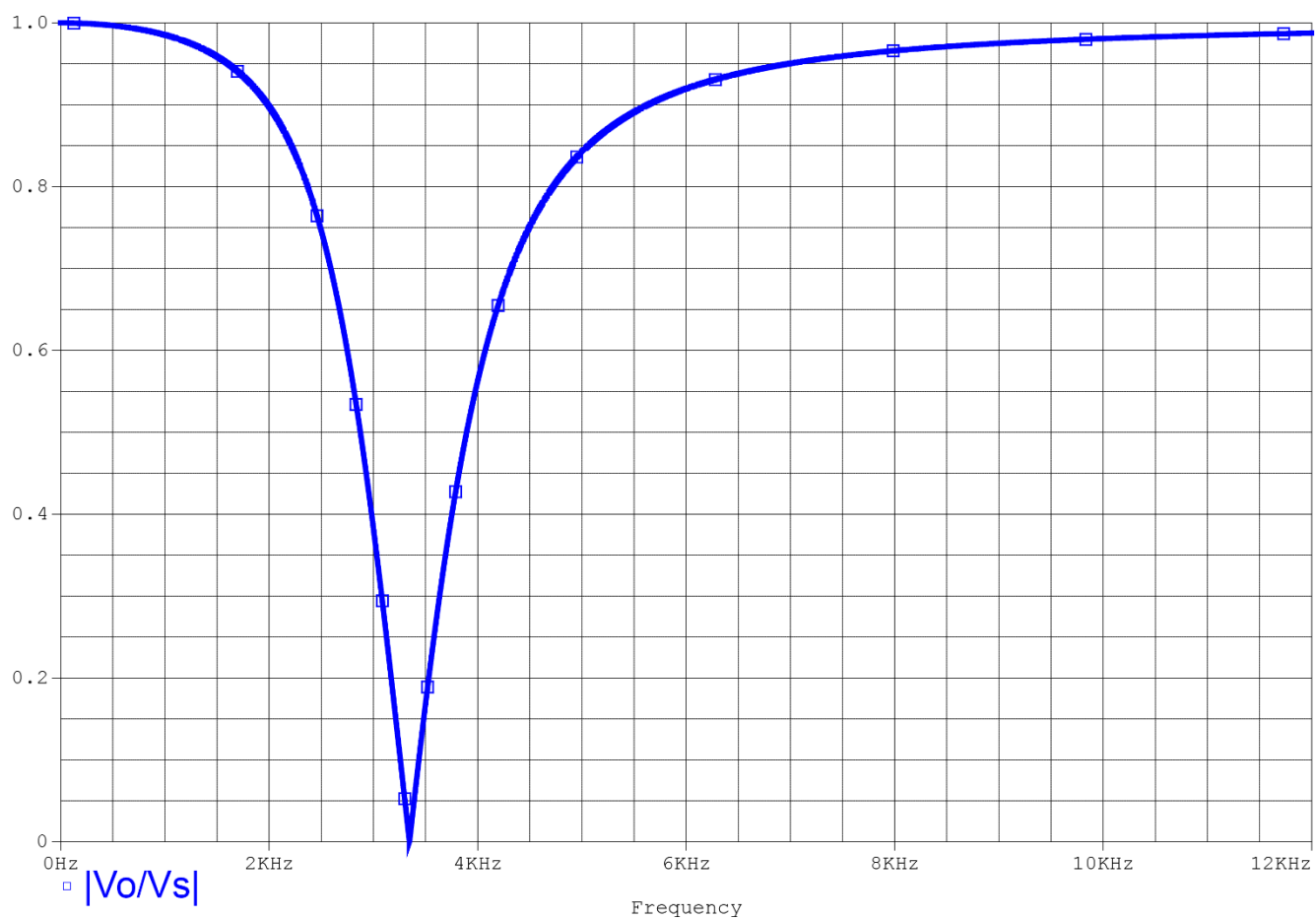


Figure 8: Magnitude of Transfer Function Using PSPICE

Appendix

%MATLAB Code

```
syms s va vi vb vc vd vo
```

```
spec = 'k.';
```

%Metric Units

```
k = 10^3;
```

```
m = 10^-3;
```

```
u = 10^-6;
```

%Plots Used In The Lab

```
H_TH(s) = (s^2 + 4.41940645 * 10^8)/(s^2 + 11087.0258*s + 4.41940645 * 10^8);
```

```
f = linspace(0,12*1000,10000);
```

```
plot(f,abs(H_TH(j*2*pi*f)))
```

```
xlabel('f [Hz]'); ylabel('Gain'); title('Gain vs Frequency');
```

```
hold on;
```

%Data Points

```
plot (1*k,985.345*m, spec)
```

```
plot (2.5*k,746.182*m, spec)
```

```
plot (3.3471*k,1.4366*m, spec)
```

```
plot (4*k,562.762*m, spec)
```

```
plot (5*k,842.613*m, spec)
```

```
plot (12*k,987.523*m, spec)
```

```
plot (2.5774*k,707.376*m, spec)
```

```
plot (4.3379*k,705.626*m, spec)
```

%Cap Values

```
C1 = .0475681*u;
```

```
C2 = .0951362*u;
```

```
ZC1 = 1/(C1*s);
```

```
ZC2 = 1/(C2*s);
```

%Definitions of nodal eqn

```
node_a = (va-vi)/ZC1 + (va-vc)/ZC1 + (va-vd)/500 == 0;
```

```
node_b = (vb-vi)/k + (vb-vc)/k + (vb)/ZC2 == 0;
```

```
node_c = (vc-va)/ZC1 + (vc-vb)/k == 0;
```

```
node_d = (vc-vd)/736.3 + (vc)/k == 0;
```

```
node_e = (vo-vd)/736.3 + (vo)/k == 0;
```

%Solving Nodal Eqn

```
sol = solve(node_a,node_b,node_c,node_d,node_e,[va,vb,vc,vd,vo]);
```

%This was done to get H(s) in a format I can compare to the lab

```
H_TEMP = (simplify(sol.vo/vi))
```

H_TEMP =

$$\frac{201841737789622195590519928784765625 s^2 + 89202980794122492566142873090593446023921664}{201841737789622195590519928784765625 s^2 + 2237872282269982398721431028295956168704 s + 89202980794122492566142873090593446023921664}$$

```
[n,d] = numden(H_TEMP)
```

n = 201841737789622195590519928784765625 s² + 89202980794122492566142873090593446023921664

d =

201841737789622195590519928784765625 s² + 2237872282269982398721431028295956168704 s + 89202980794122492566142873090593446023921664

```
H_num = vpa(n/201841737789622195590519928784765625,4)
```

H_num = 1.0 s² + 4.419e+8

```
H_den = vpa(d/201841737789622195590519928784765625,4)
```

H_den = 1.0 s² + 11090.0 s + 4.419e+8

```
H(s) = (s^2 + 4.419e+8)/(s^2 + 11090 *s + 4.419e+8)
```

H(s) =

$$\frac{s^2 + 441900000}{s^2 + 11090 s + 441900000}$$